

SI-2026 Analog IC Design Review: Circuits



28-29 May 2026

2. Draw the output wave form of the below figure for a pulse input.



a) $RC \ll T$

b) $RC \gg T$

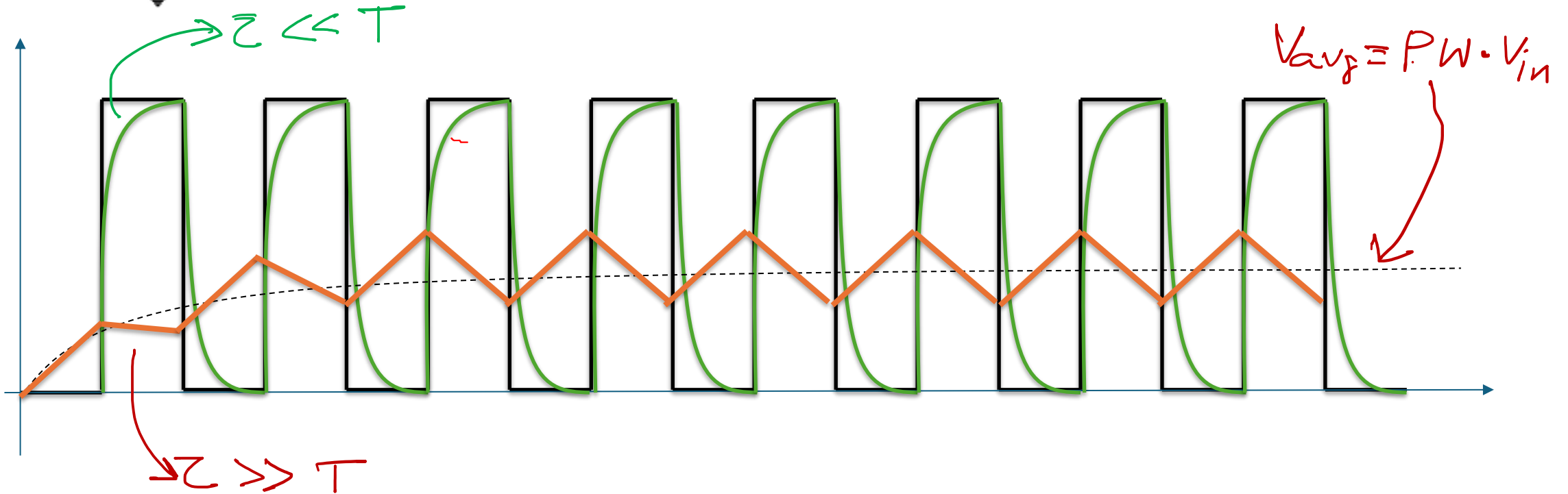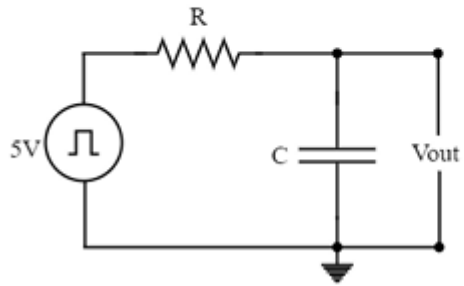
c) Find the average output voltage for the above two cases.



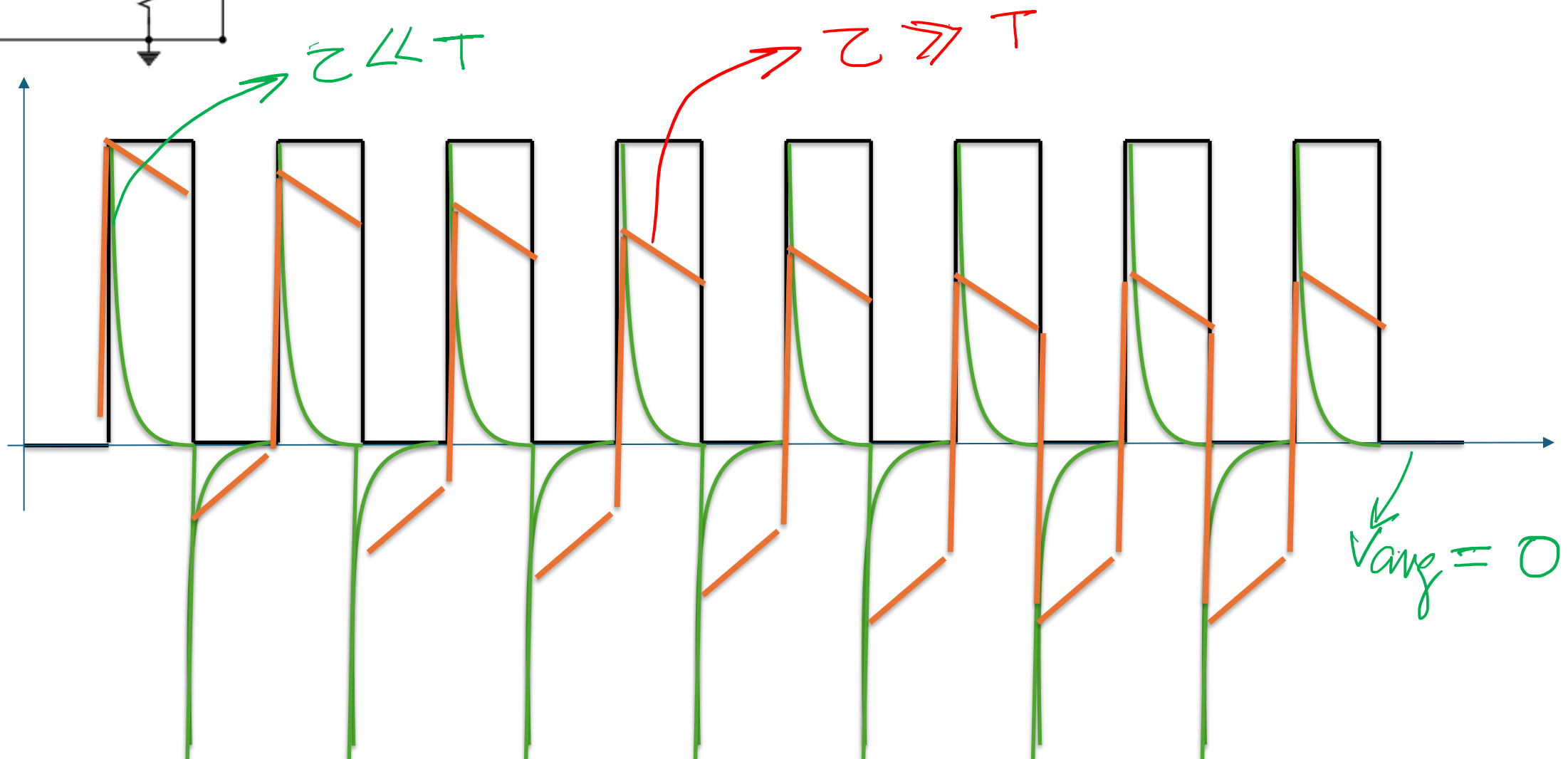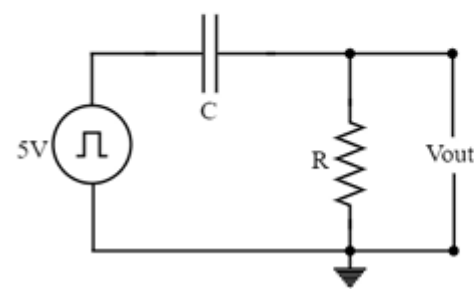4. Draw the output wave form of the below figure for a pulse input.
- d) $RC \ll T$
 - e) $RC \gg T$
 - f) Find the average output voltage for the above two cases.



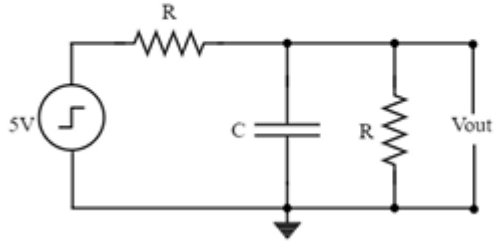5. Draw the step response of the below circuit diagram.



① Determine the order: 1^{st} order

② Type: RC (low pass) or CR (HPF): RC/LPF

③ Initial value: 0


④ Final value: $V_{in}/2 = 2.5V$

⑤ $\tau = R_{eq}C = R/2 \cdot C$



↳ Follow open-circuit time constant

① All independent source = 0

② R_{eq} in parallel to C

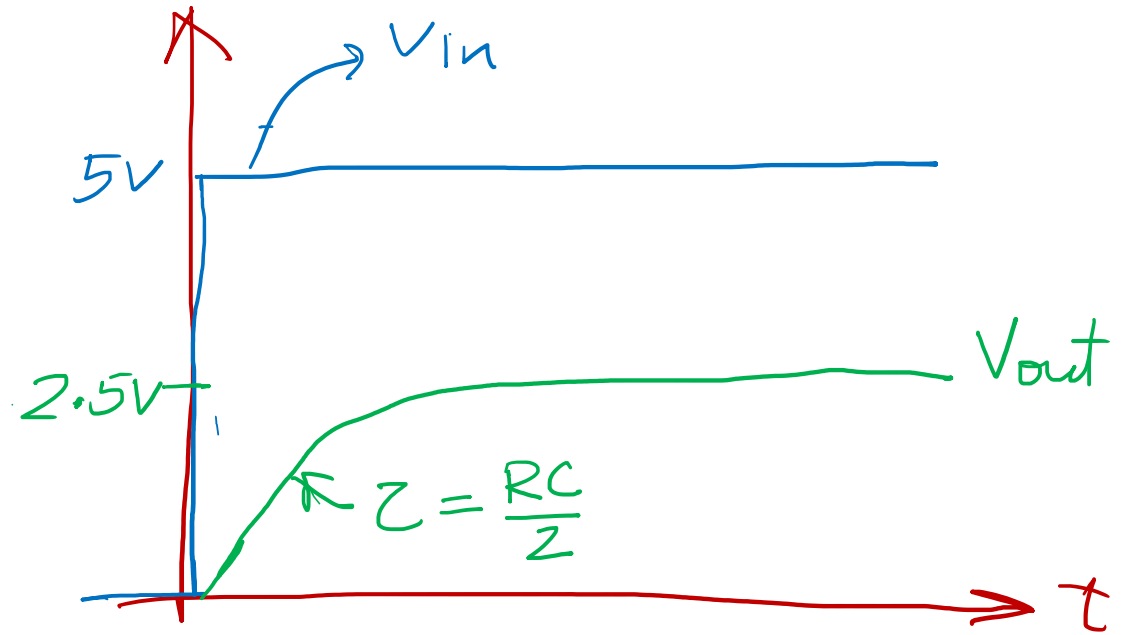


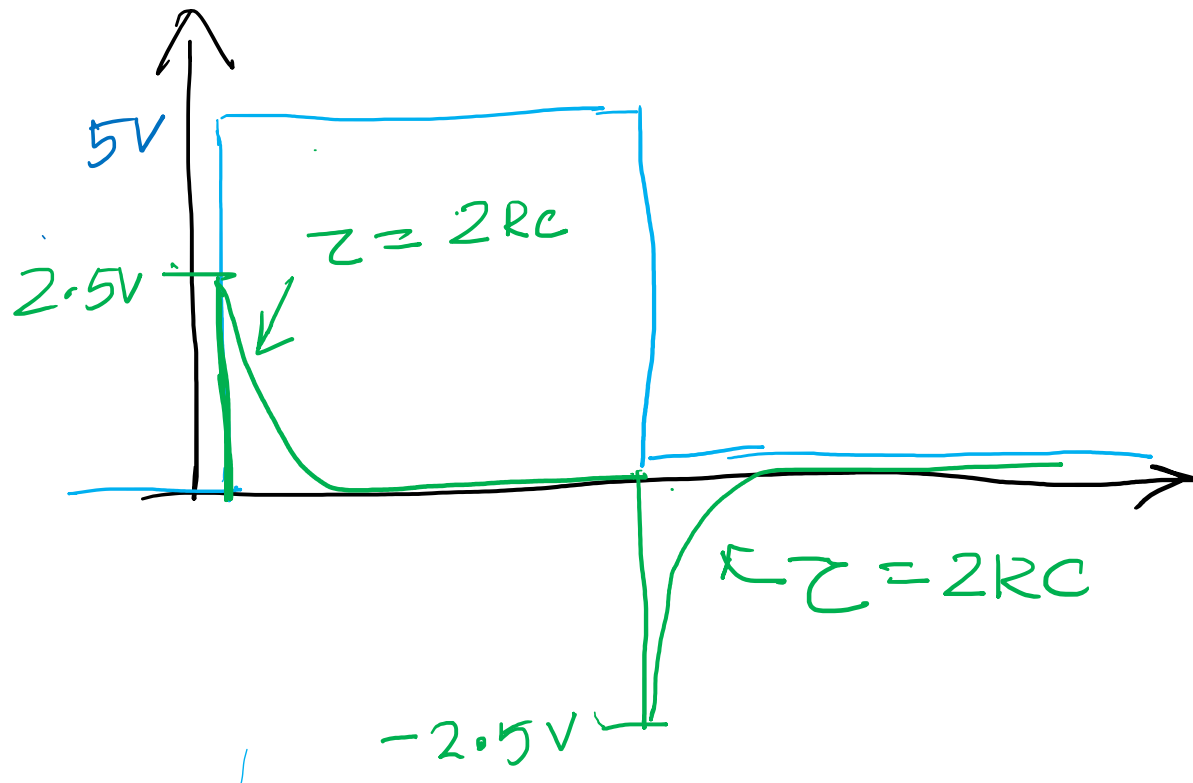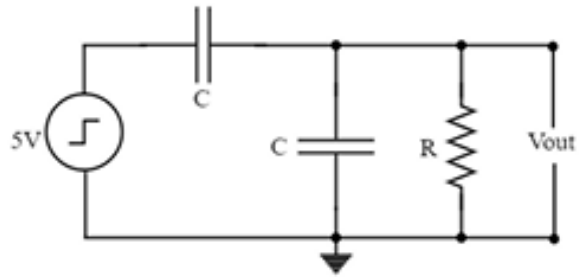6. Draw the step response of the below circuit diagram.




Active Circuits

• Linear Dependent Sources

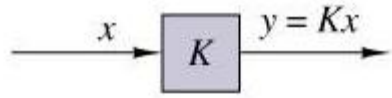


(a)

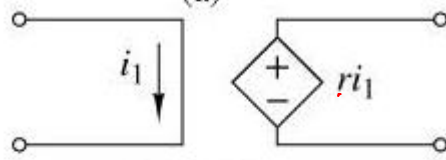


(b) CCVS

Transimpedance amplifier

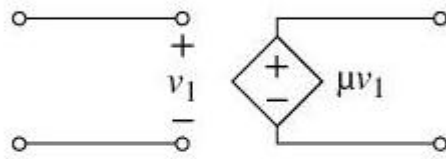

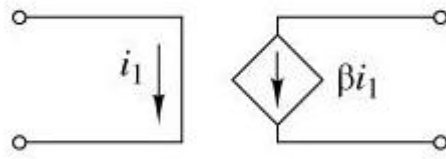
(c) VCVS

Voltage amplifier (opamp can be modeled w/ this)



(d) CCCS


Current amplifier

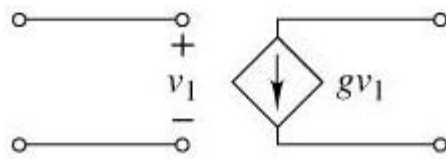

(e) VCCS

Transconductance amplifier (OTAs can be modeled)

- Analysis using Dependent Sources

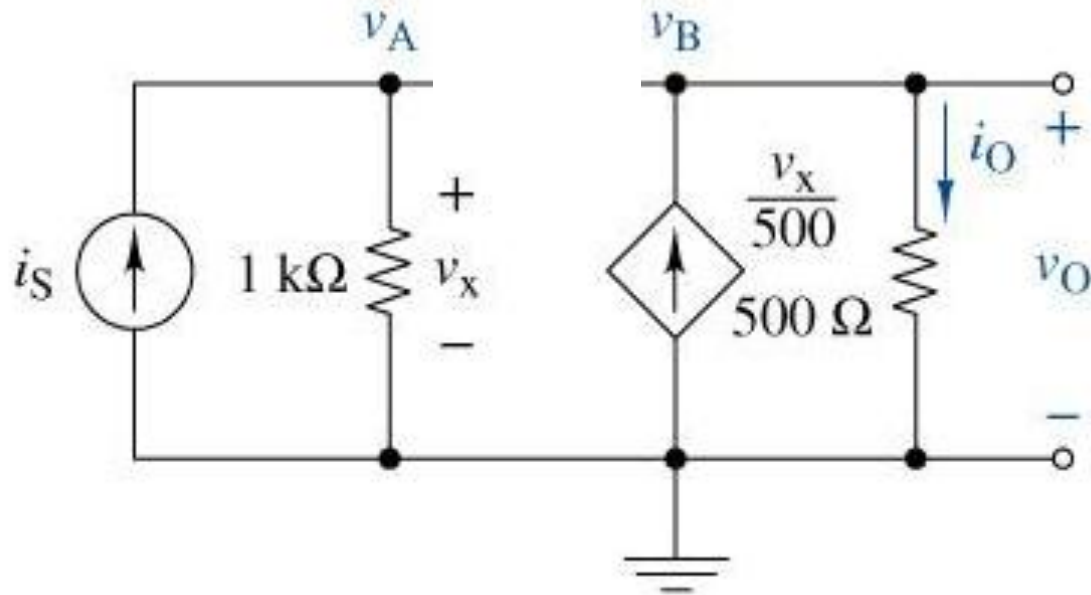



$$V_o = i_o \cdot R_o$$

$$= \frac{V_x}{500} \times 500$$



$$= i_S \cdot 1\text{ k}\Omega$$

$$\frac{V_o}{i_S} = 1\text{ k}\Omega$$

- Operational Amplifier Model

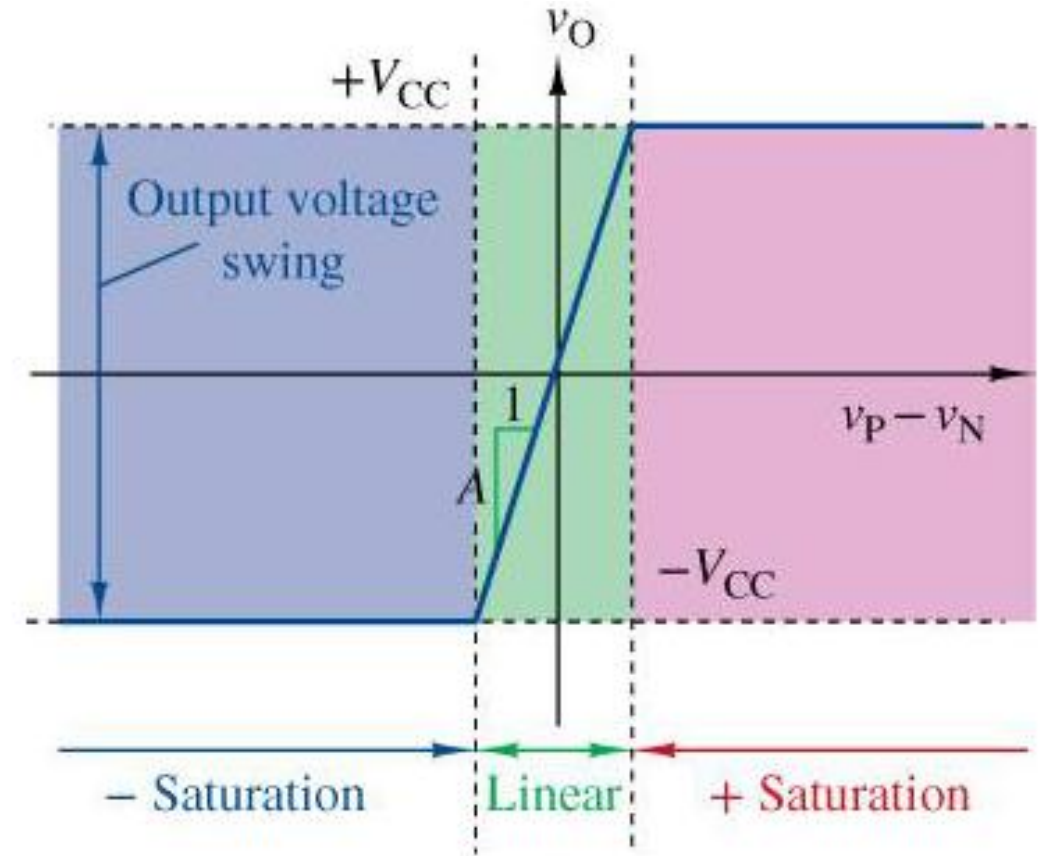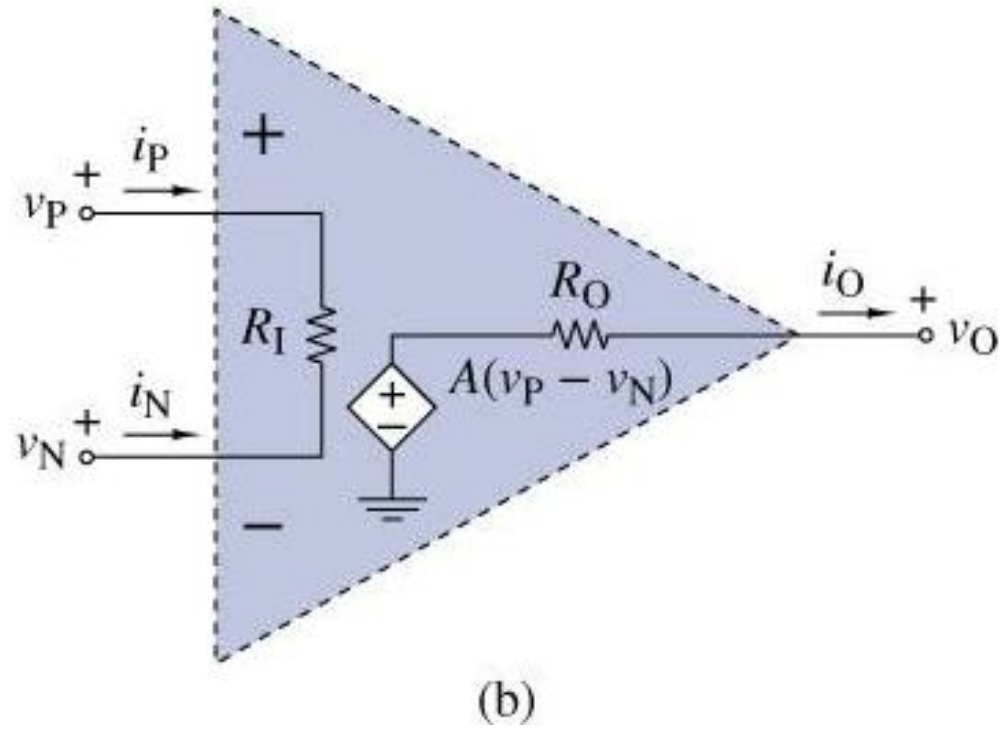


• Operational Amplifier Analysis

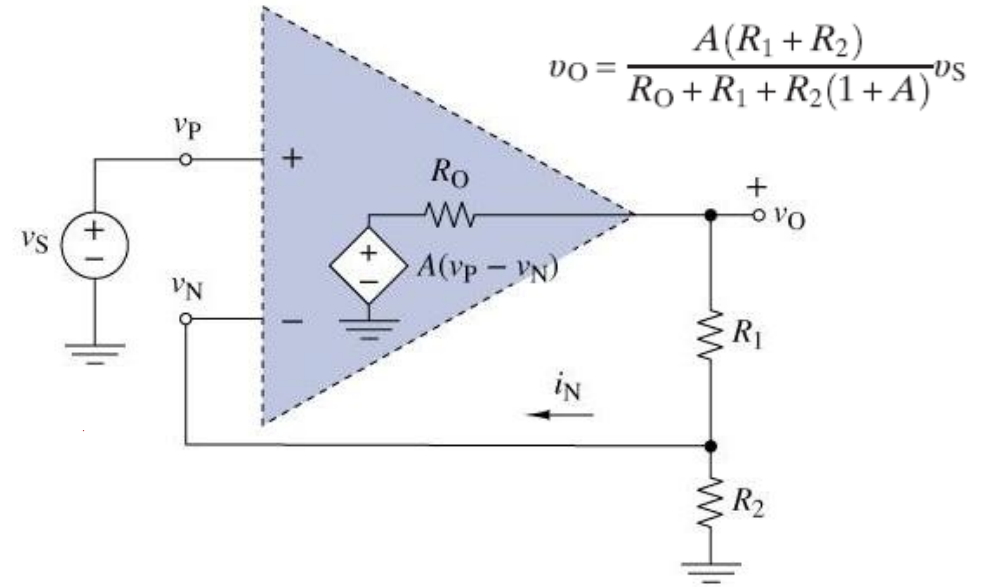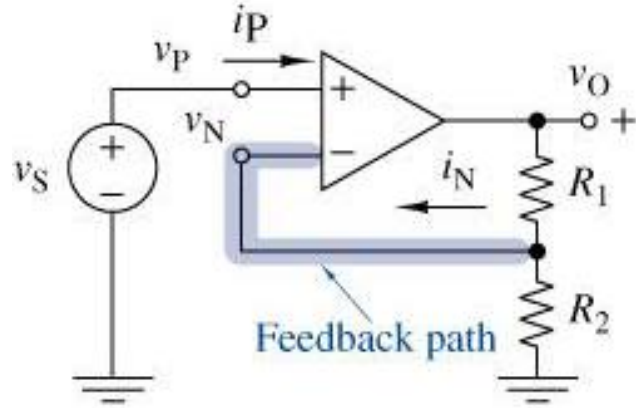

In ideal case $R_O = 0$ & $A = \infty$

$$\frac{v_O}{v_S} = \frac{R_1 + R_2}{\frac{R_O}{A} + \frac{R_1}{A} + R_2 \left(\frac{1}{A} + 1 \right)} = 1 + \frac{R_1}{R_2}$$

• Operational Amplifier Analysis

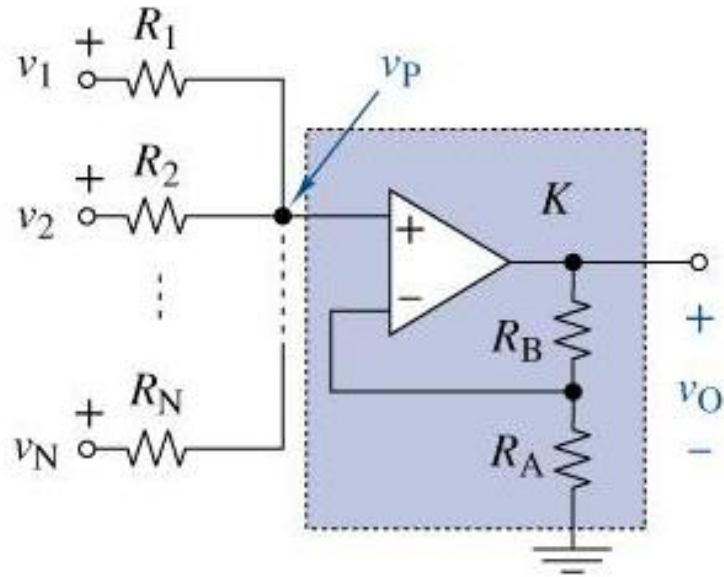


$$\frac{v_O}{v_P} = 1 + \frac{R_B}{R_A}$$

$$\frac{v_P}{v_1} = \frac{R_2 \parallel R_3 \parallel \dots \parallel R_N}{\sum R_k}$$

$$\frac{v_O}{v_2} = \frac{R_1 \parallel R_3 \parallel \dots \parallel R_N}{\sum R_k}$$

By superposition:










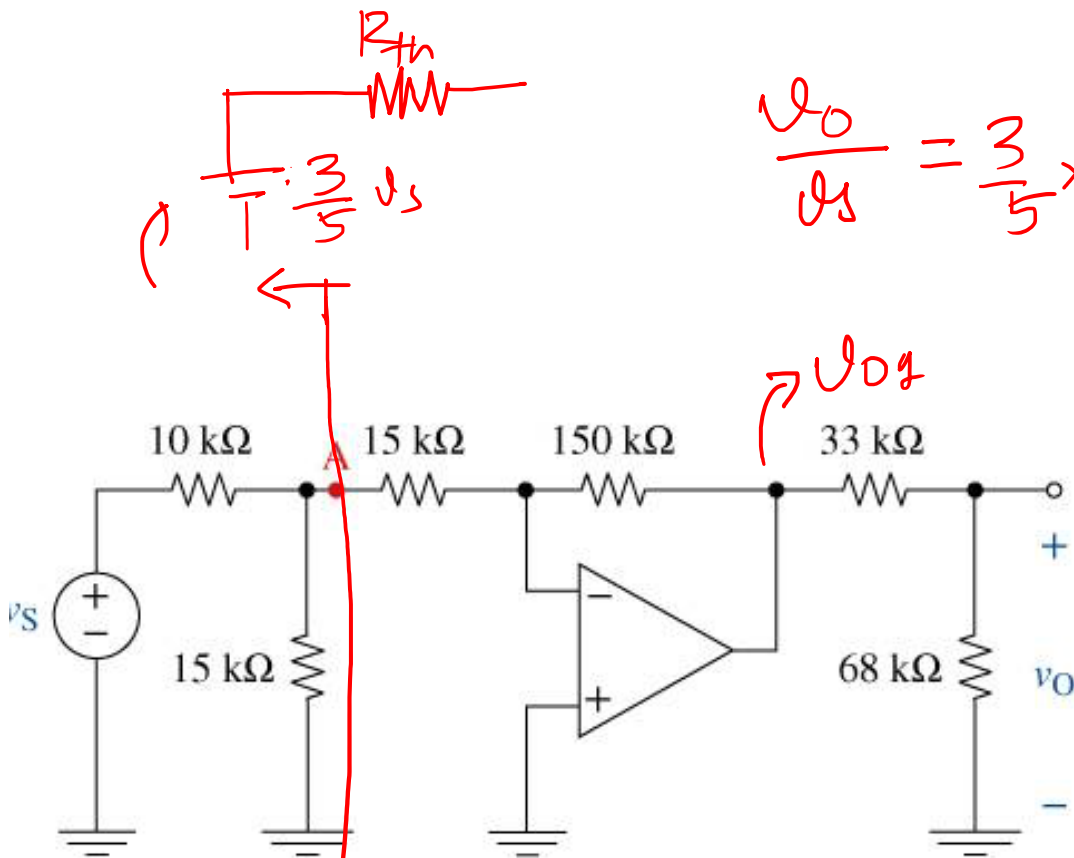
$$\left(\frac{v_O}{v_1} + \frac{v_O}{v_2} + \dots \right)$$







$$\frac{v_O}{v_S} = \frac{3}{5} \times -\frac{150k}{21k} \times \frac{68k}{(68+33)k} = -\frac{30}{7} \times \frac{68}{101} = \underline{\underline{-2.88}}$$


Thevenin equiv.

$$V_{TH} = v_S \times \frac{15}{25} = \frac{3}{5} v_S \quad \left| \quad R_{TH} = \frac{15k \times 10k}{15k + 10k} = 6 k\Omega \right.$$

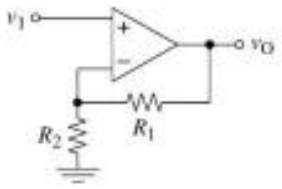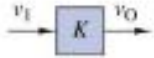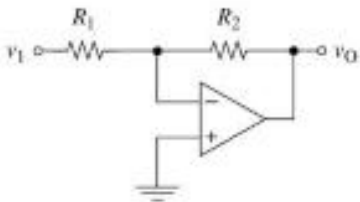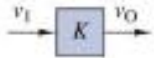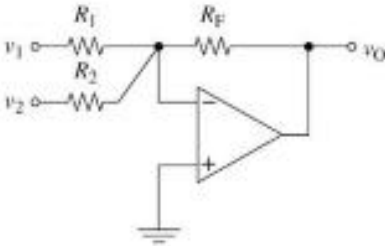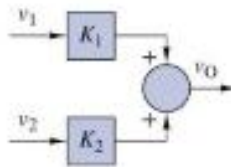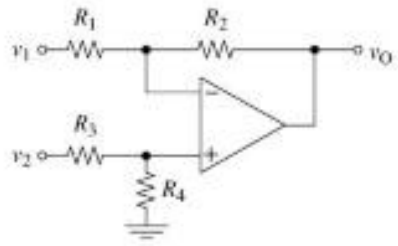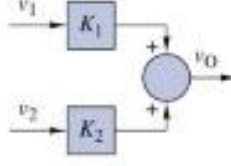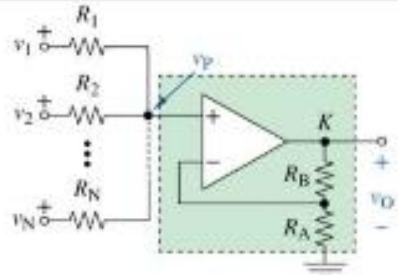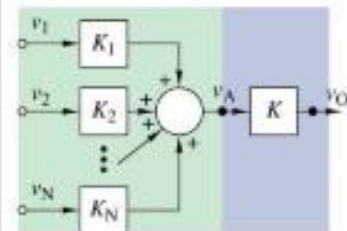
Circuit	Block diagram	Gains
	Non Inverting 	$K = \frac{R_1 + R_2}{R_2}$
	Inverting 	$K = -\frac{R_2}{R_1}$
	Inverting Summer 	$K_1 = -\frac{R_F}{R_1}$ $K_2 = -\frac{R_F}{R_2}$
	Subtractor 	$K_1 = -\frac{R_2}{R_1}$ $K_2 = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right)$
	Non-Inverting Summer 	$K = \frac{R_B + R_A}{R_A}$ $K_1 = \frac{(R_2 \parallel R_3 \parallel \dots \parallel R_N)}{R_1 + (R_2 \parallel R_3 \parallel \dots \parallel R_N)}$ $K_N = \frac{(R_1 \parallel R_2 \parallel \dots \parallel R_{N-1})}{R_N + (R_1 \parallel R_2 \parallel \dots \parallel R_{N-1})}$

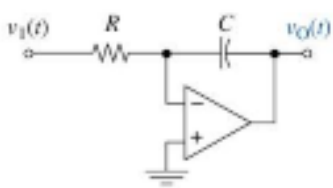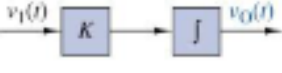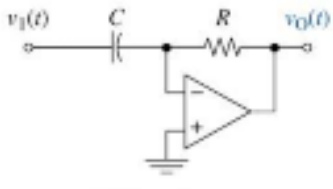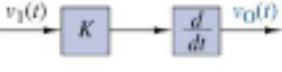 Integrator		$K = -\frac{1}{RC}$
 Differentiator		$K = -RC$


• Capacitance

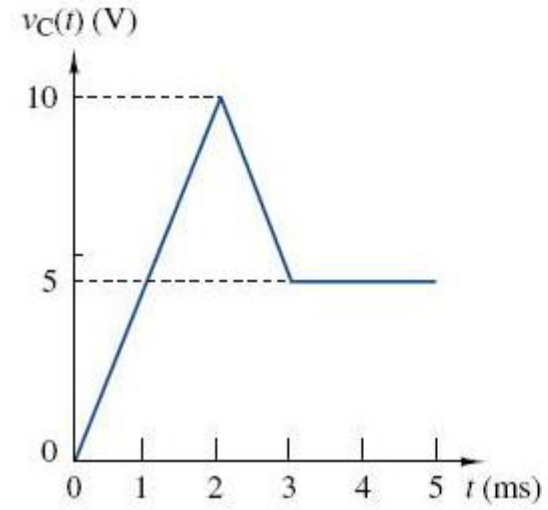


(a)

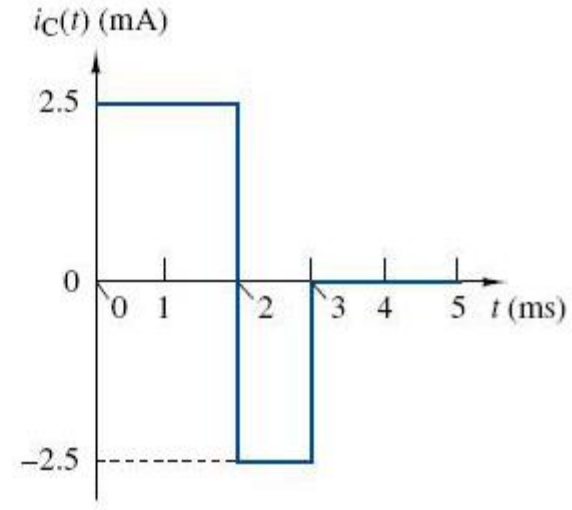

(b)




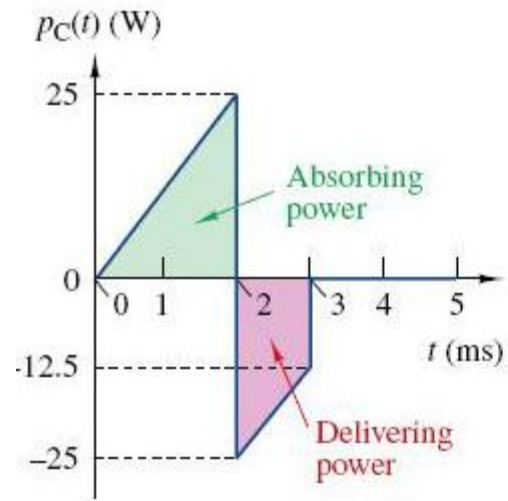


(c)

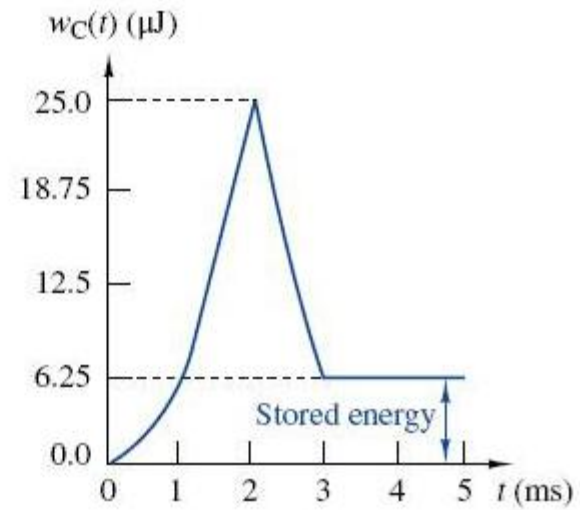


(d)

• **First-Order Circuits**

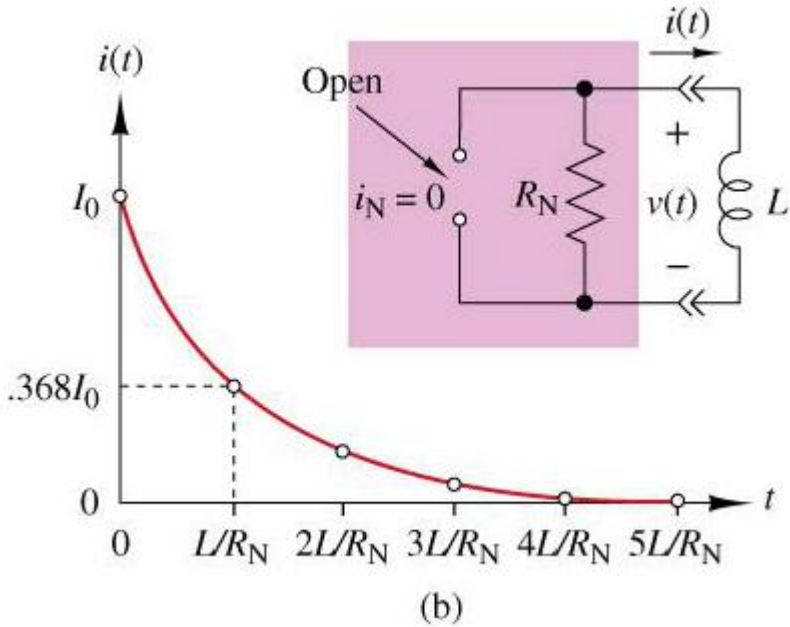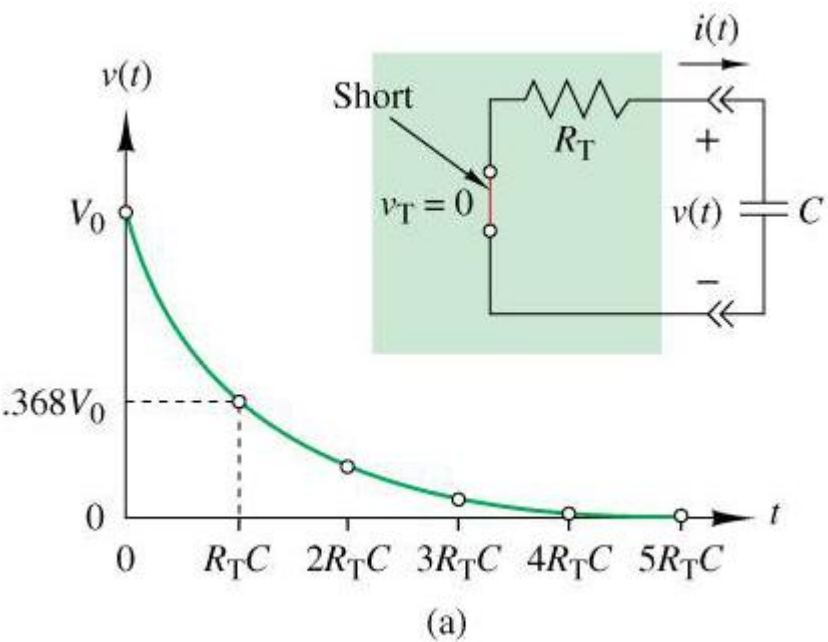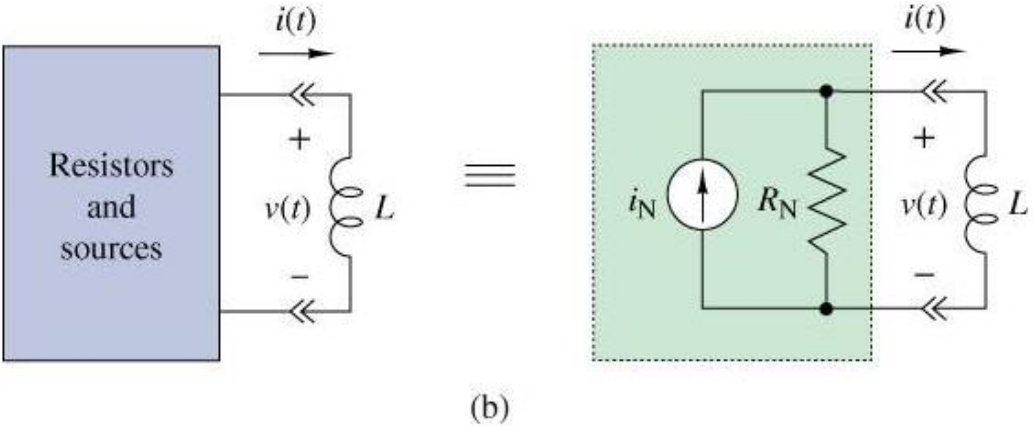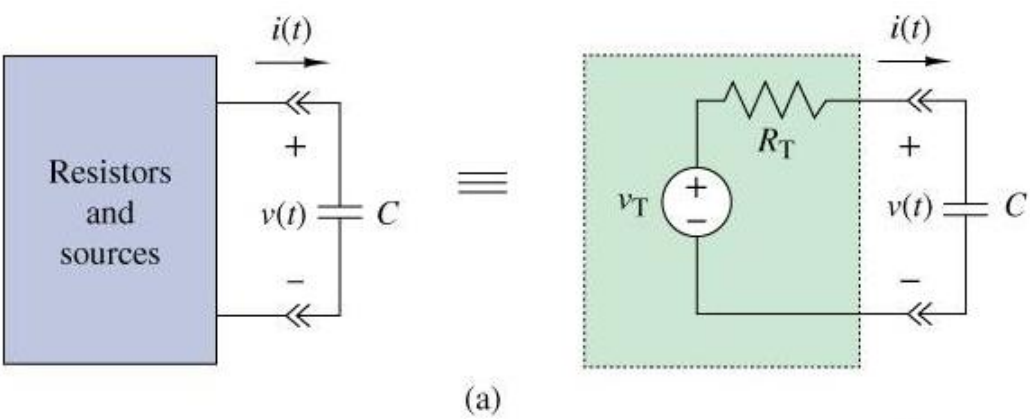

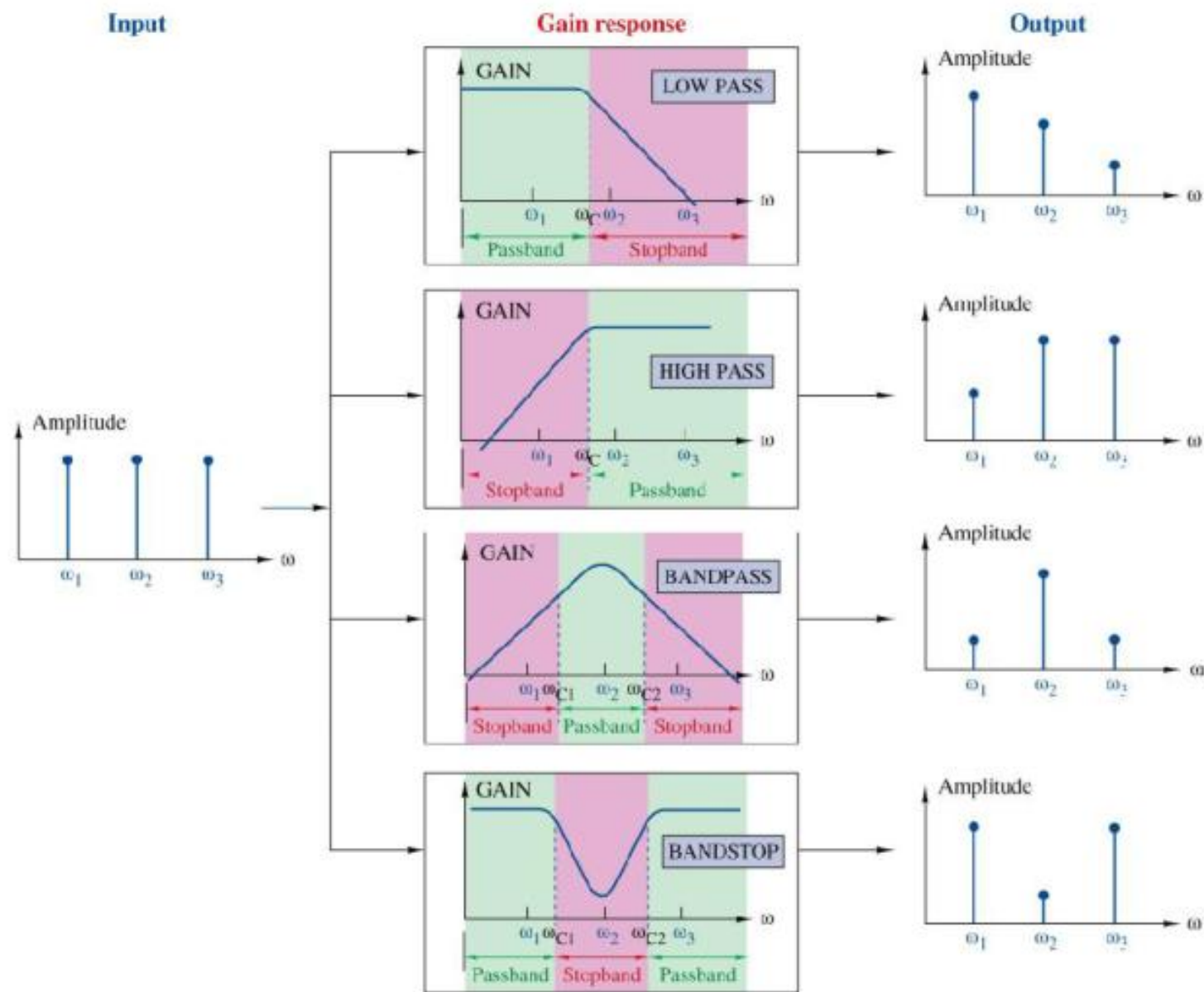• Frequency Response (Four Basic Gain Responses)



• First-Order Low-Pass Response


$$T(s) = \frac{K}{s + \alpha}$$

$$T(j\omega) = \frac{K}{j\omega + \alpha}$$

$$|T(j\omega)| = \frac{|K|}{\sqrt{\omega^2 + \alpha^2}}$$

$$\theta(\omega) = angle(K) - \tan^{-1}(\omega/\alpha)$$

$ T(j\omega) $	$ T(j\omega) _{dB}$
10^3	60
10^2	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
0.5	-6
10^{-1}	-20
10^{-2}	-40
10^{-3}	-60

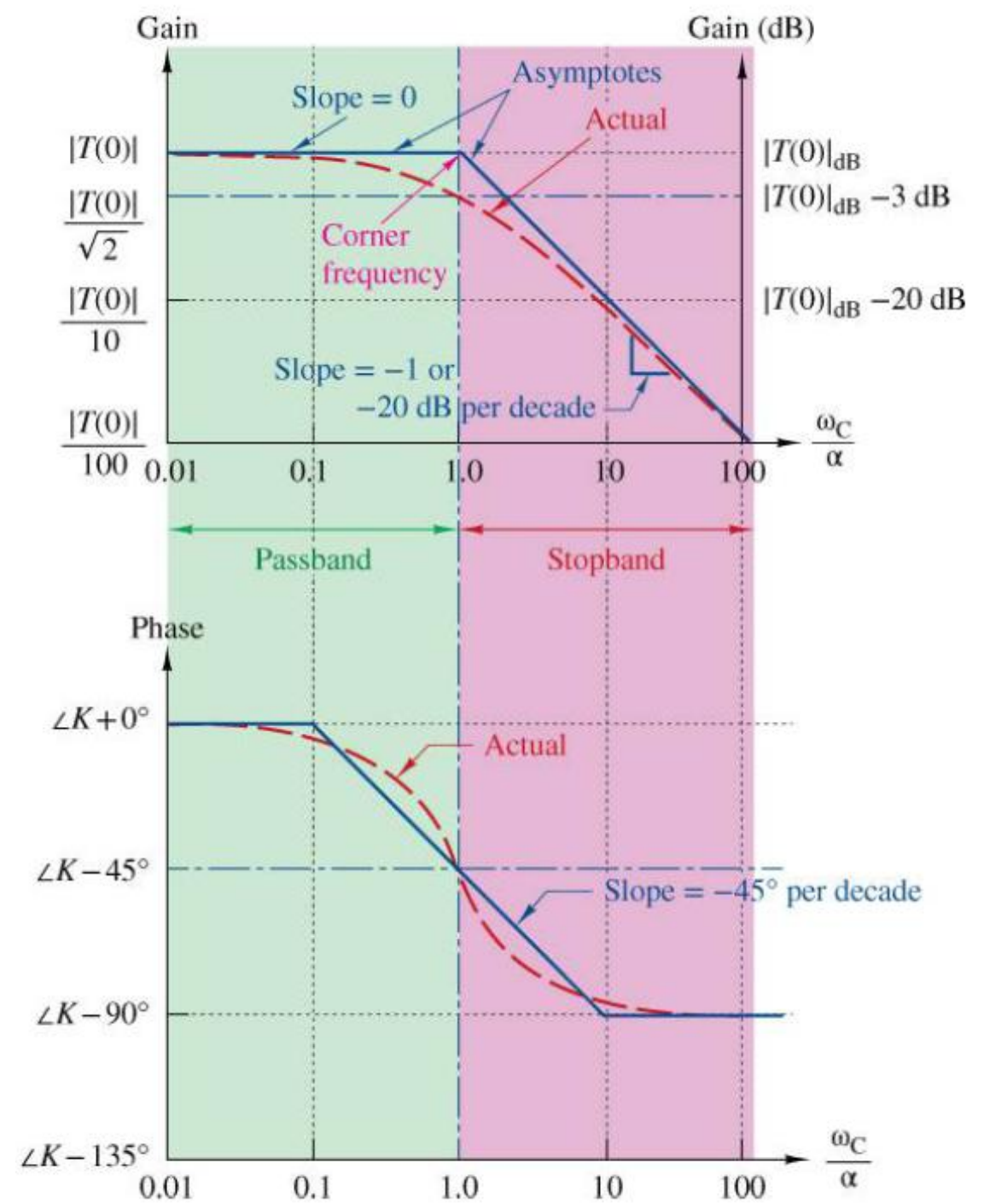


• First-Order High-Pass Response

$$T(s) = \frac{Ks}{s + \alpha}$$


$$T(j\omega) = \frac{j\omega K}{j\omega + \alpha}$$

$$|T(j\omega)| = \frac{|K|\omega}{\sqrt{\omega^2 + \alpha^2}}$$

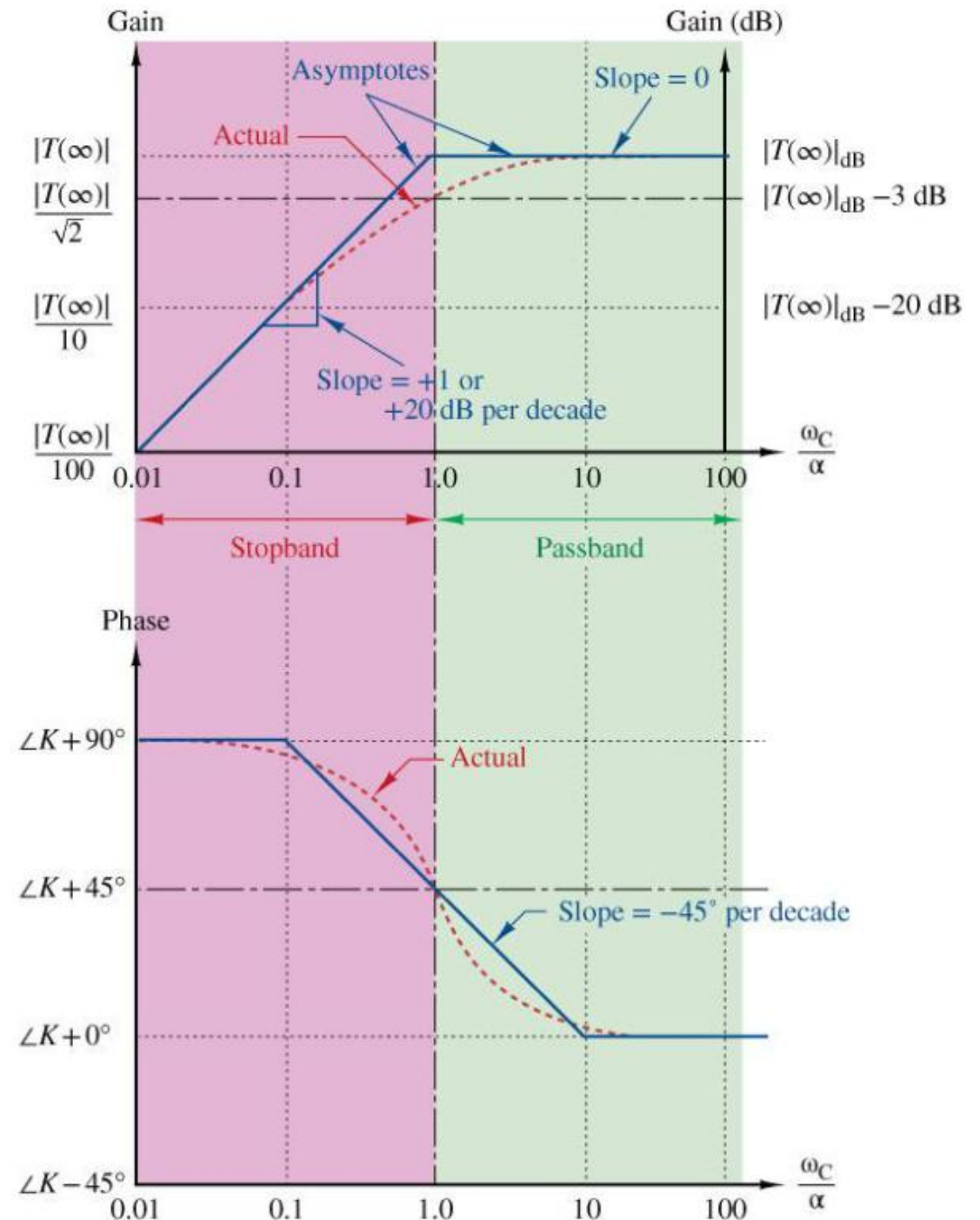
$$\theta(\omega) = \text{angle}(K) + 90^\circ - \tan^{-1}(\omega/\alpha)$$




(a)

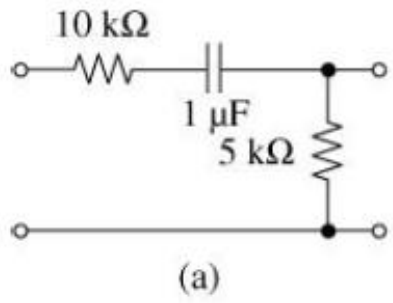


(a)

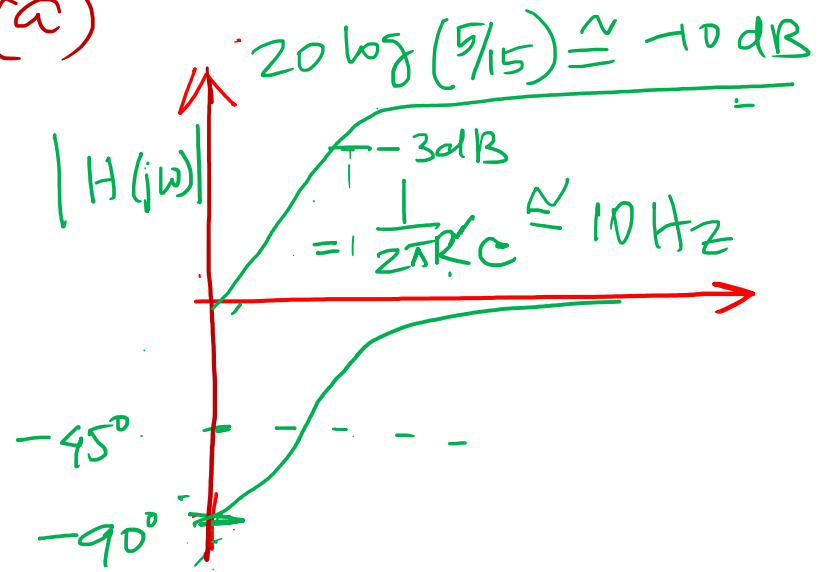


(b)

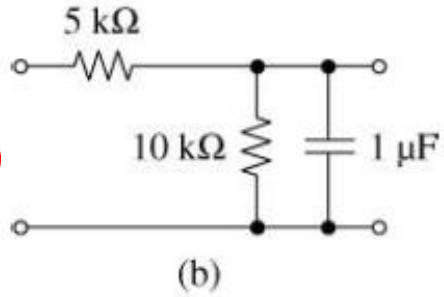


(b)

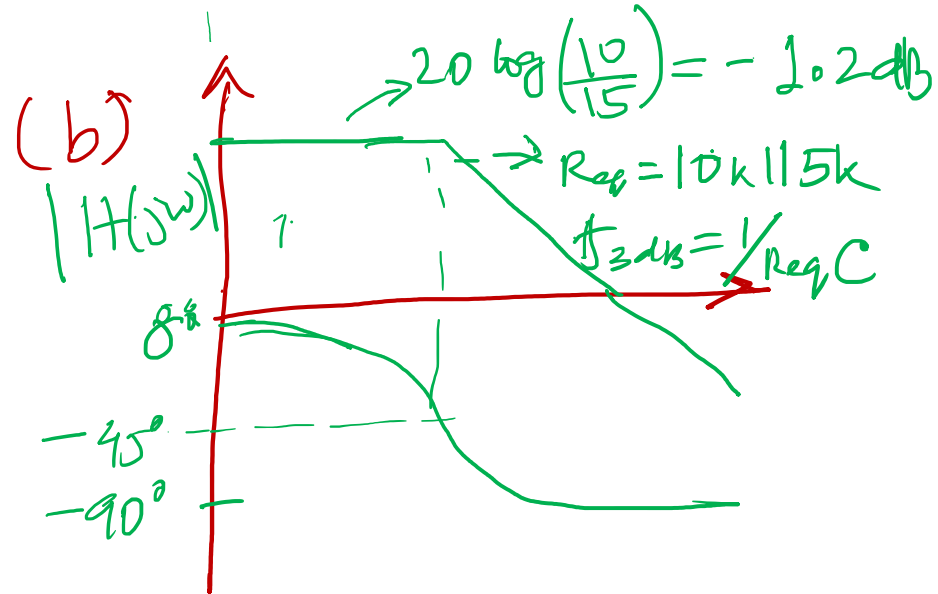


(c)

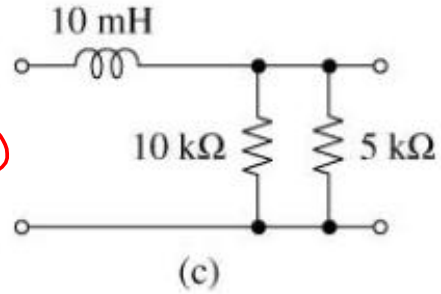

(d)

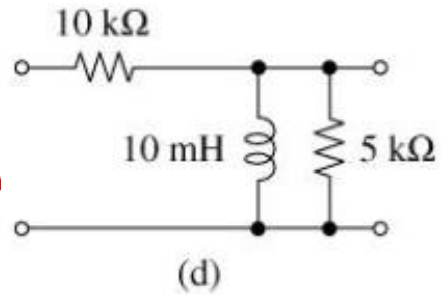


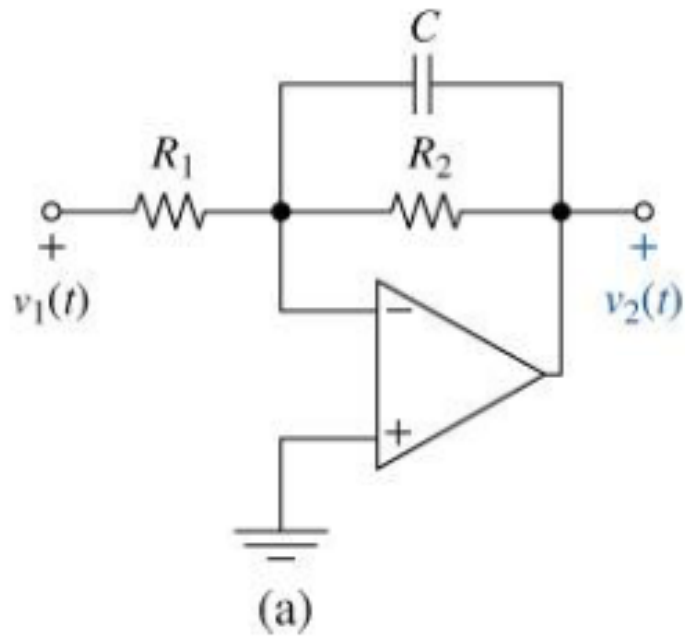

→ LPF;

$$\text{Gain} = -\frac{R_2}{R_1}$$

$$\text{pole} = \frac{1}{2\pi R_2 C}$$


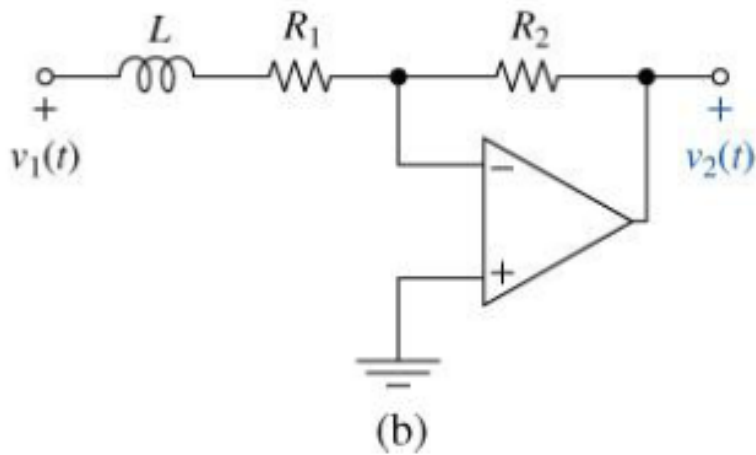


LPF

$$\text{Gain} = -\frac{R_2}{R_1}$$

$$\text{pole} = \frac{1}{R_1}$$

• First-Order Band-Pass Response

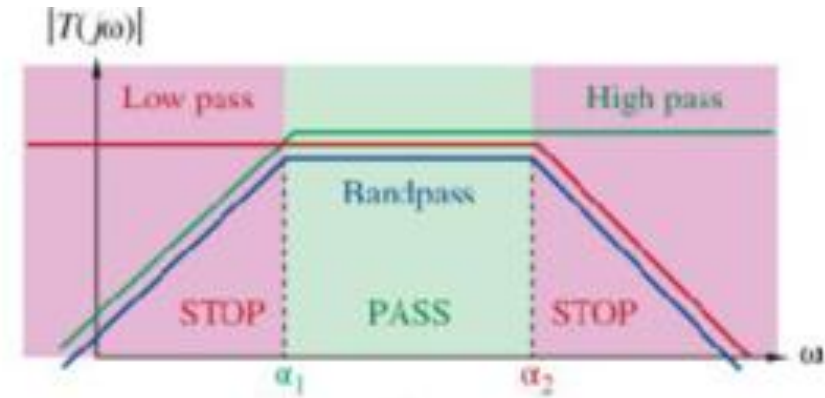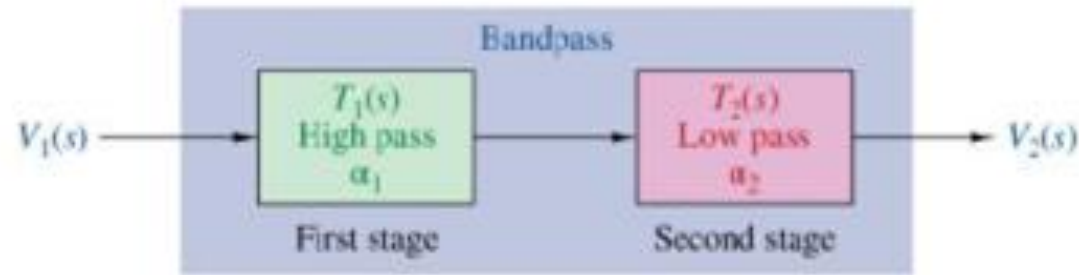

$$T(s) = T_1(s) \times T_2(s) = \underbrace{\left(\frac{K_1 s}{s + \alpha_1} \right)}_{\text{high pass}} \underbrace{\left(\frac{K_2}{s + \alpha_2} \right)}_{\text{low pass}}$$

Low frequency ($\omega \ll \alpha_1 \ll \alpha_2$): $|T(j\omega)| \rightarrow \underbrace{\left(\frac{|K_1|\omega}{\alpha_1} \right)}_{\text{high pass}} \underbrace{\left(\frac{|K_2|}{\alpha_2} \right)}_{\text{low pass}} = \frac{|K_1||K_2|\omega}{\alpha_1 \alpha_2}$

$$|T(j\omega)| = \underbrace{\left(\frac{|K_1|\omega}{\sqrt{\omega^2 + \alpha_1^2}} \right)}_{\text{high pass}} \underbrace{\left(\frac{|K_2|}{\sqrt{\omega^2 + \alpha_2^2}} \right)}_{\text{low pass}}$$

High frequency ($\alpha_1 \ll \alpha_2 \ll \omega$): $|T(j\omega)| \rightarrow \underbrace{\left(\frac{|K_1|\omega}{\omega} \right)}_{\text{high pass}} \underbrace{\left(\frac{|K_2|}{\omega} \right)}_{\text{low pass}} = \frac{|K_1||K_2|}{\omega}$

Mid-frequency ($\alpha_1 \ll \omega \ll \alpha_2$): $|T(j\omega)| \rightarrow \underbrace{\left(\frac{|K_1|\omega}{\omega} \right)}_{\text{high pass}} \underbrace{\left(\frac{|K_2|}{\alpha_2} \right)}_{\text{low pass}} = \frac{|K_1||K_2|}{\alpha_2}$